



KUNGL. TEKNISKA HÖGSKOLAN

CMOS Arithmetic Circuits


Prof. Hannu Tenhunen
Royal Institute of Technology
Department of Electronics
Electronic System Design Laboratory
hannu@ele.kth.se

KTH/ESDlab/HT

10/4/00

1

Arithmetic datapath role

 

KTH/ESDlab/HT

10/4/00

2

Building blocks for digital architectures

- ◆ Arithmetic unit
 - bit-sliced datapath (adder, multiplier, shifter, comparator)
 - bit-serial datapaths (adder, multiplier, shifter, comparator)
- ◆ Memory
 - RAM, ROM, buffers, shift registers
- ◆ Control
 - finite state machines (PLA, random logic)
 - counters
- ◆ Interconnect
 - switches
 - arbiters
 - bus

KTH/ESDlab/HT

10/4/00

3

Binary number representations


KTH/ESDlab/HT

10/4/00

4

Number systems: sign and magnitude

Sign and Magnitude Representation

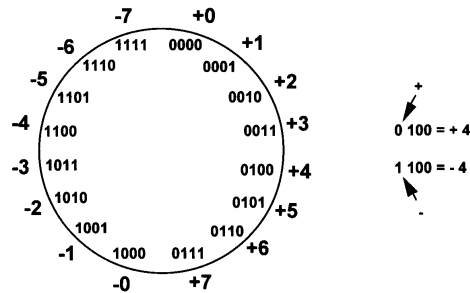

High order bit is sign: 0 = positive (or zero), 1 = negative

Three low order bits is the magnitude: 0 (000) thru 7 (111)

Number range for n bits = $\pm 2^{n-1} - 1$

Representations for 0


KTH/ESDlab/HT

10/4/00

5

Number systems: one's complement

Ones Complement

 

Subtraction implemented by addition & 1's complement

Still two representations of 0! This causes some problems

Some complexities in addition

KTH/ESDlab/HT


10/4/00

6

Number systems: two's complement

Twos Complement

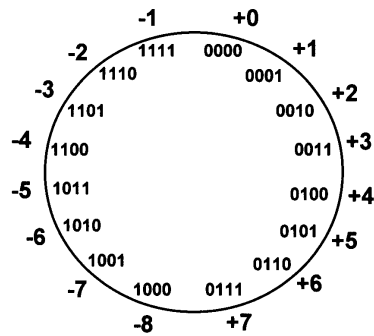*like 1's comp
except shifted
one position
clockwise*



$0\ 100 = +4$
 $1\ 100 = -4$

Only one representation for 0

One more negative number than positive number

KTH/ESDlab/HT

10/4/00

7

Addition and subtraction of numbers

Twos Complement Calculations

4	0100	-4	1100
+ 3	0011	+ (-3)	1101
7	0111	-7	11001

If carry-in to sign =
carry-out then ignore
carry

if carry-in differs from
carry-out then overflow

4	0100	-4	1100
- 3	1101	+ 3	0011
1	10001	-1	1111

Simpler addition scheme makes twos complement the most common
choice for integer number systems within digital systems

KTH/ESDlab/HT

10/4/00

8


Multiplication of numbers

Partial Product Accumulation

				A3	A2	A1	A0
				B3	B2	B1	B0
				A2 B0	A2 B0	A1 B0	A0 B0
			A3 B1	A2 B1	A1 B1	A0 B1	
		A3 B2	A2 B2	A1 B2	A0 B2		
	A3 B3	A2 B3	A1 B3	A0 B3			
S7	S6	S5	S4	S3	S2	S1	S0

Datapath circuit techniques for adders

Binary adder

 


A	B	C_i	S	C_o	<i>Carry status</i>
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

KTH/ESDlab/HT

10/4/00

11

Binary adder

 

Define 3 new variable which ONLY depend on A, B

Generate (G) = AB

Propagate (P) = $A \oplus B$

Delete = $\bar{A} \bar{B}$

$$S = A \oplus B \oplus C_i$$

$$= A\bar{B}\bar{C}_i + \bar{A}B\bar{C}_i + \bar{A}\bar{B}C_i + ABC_i$$

$$C_o = AB + BC_i + AC_i$$

$$C_o(G, P) = G + PC_i$$


$$S(G, P) = P \oplus C_i$$

KTH/ESDlab/HT

10/4/00

12

Ripple carry adder

 

Worst case delay linear with the number of bits

$$t_d = O(N)$$

$$t_{adder} \approx (N-1)t_{carry} + t_{sum}$$


Goal: Make the fastest possible carry path circuit

KTH/ESDlab/HT

10/4/00

13

CMOS full adder

 

28 Transistors

KTH/ESDlab/HT

10/4/00

14

Dynamic NP-CMOS full adder

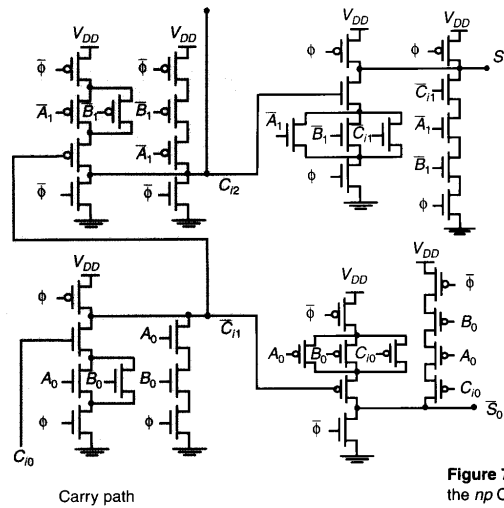


Figure 7.9 Dynamic full adder using the *np*-CMOS logic style.

KTH/ESDlab/HT

10/4/00

15

Dynamic NP-CMOS full adder

 


Figure 7.10 Layout of dynamic full adder using the *np*-CMOS logic style (from [Kleinfelder91]).

KTH/ESDlab/HT

10/4/00

16

Pipelined adder

 



Figure 7.14 Pipelined adder in NOR-CMOS (showing only bit i and bit $i + 1$).

KTH/ESDlab/HT

10/4/00

17

Carry bypass adder

 

Idea: If (P_0 and P_1 and P_2 and $P_3 = 1$)
then $C_{03} = C_0$, else "kill" or "generate".

KTH/ESDlab/HT

10/4/00

18

Carry bypass adder

 



Figure 7.18 Propagation delay of ripple-carry versus carry-bypass adder.

KTH/ESDlab/HT

10/4/00

19

Linear carry select adder

 


KTH/ESDlab/HT

10/4/00

20

Linear carry select adder: critical path

 

$$t_{add} = t_{setup} + \left(\frac{N}{M}\right)t_{carry} + Mt_{mux} + t_{sum}$$

KTH/ESDlab/HT

10/4/00

21

Carry look-ahead adder

• THE SIGNALS ASSOCIATED WITH THE ADDER ARE:

GENERATE SIGNAL G_i

$$G_i = A_i \cdot B_i$$

PROPAGATE SIGNAL P_i

$$P_i = A_i + B_i$$

CARRY SIGNAL C_i

$$C_i = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i \dots P_1 C_0$$

SUM SIGNAL S_i

$$S_i = C_{i-1} \oplus A_i \oplus B_i$$

For four stages

$$C_1 = G_1 + P_1 C_0$$


$$C_2 = G_2 + P_2 G_1 + P_2 P_1 C_0$$

$$C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 C_0$$

$$C_4 = G_4 + P_4 G_3 + P_4 P_3 G_2 + P_4 P_3 P_2 G_1 + P_4 P_3 P_2 P_1 C_0$$

$$= G_4 + P_4 \cdot (G_3 + P_3 \cdot (G_2 + P_2 \cdot (G_1 + P_1 \cdot C_0)))$$

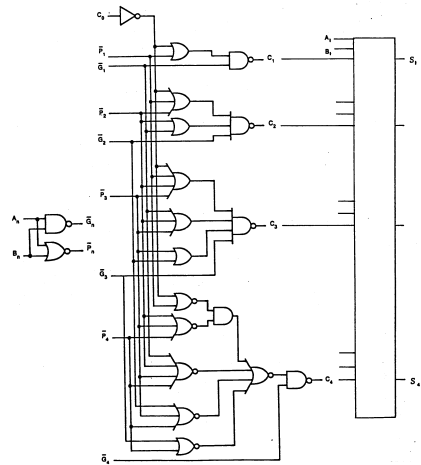• THE FOLLOWING IS A SCHEMATIC OF A 4-BIT LOOKAHEAD ADDER WITH GATES DECOMPOSED TO YIELD GATES WITH A MAXIMUM OF FOUR TRANSISTORS IN SERIES.




KTH/ESDlab/HT

10/4/00


22

Carry look-ahead circuit structures


• Static carry lookahead gate

 

• A REPRESENTATIVE LAYOUT IS SHOWN BELOW

 

• Domino carry lookahead

 


KTH/ESDlab/HT

10/4/00

23

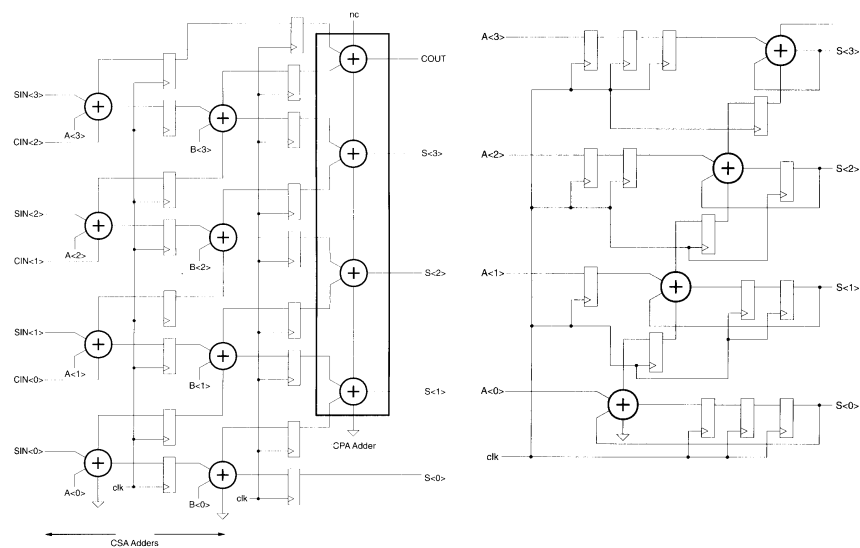Carry save (CSA) and carry propagate (CPA) adders




KTH/ESDlab/HT

10/4/00

24

Adder delays

 


KTH/ESDlab/HT

10/4/00



25

Adder delays summary

● Carry-Look-Ahead Adder

 

■ Carry Select Adder

  

KTH/ESDlab/HT

10/4/00

26

Datapath circuit techniques for multipliers

KTH/ESDlab/HT

10/4/00

27

Multiplier definition

Consider two *unsigned* binary numbers X and Y that are M and N bits wide respectively. To introduce the multiplication operation, it is useful to express X and Y in a binary representation.

$$X = \sum_{i=0}^{M-1} X_i 2^i \quad Y = \sum_{j=0}^{N-1} Y_j 2^j \quad (7.23)$$

with $X_i, Y_j \in \{0, 1\}$. The multiplication operation is then defined as follows:

$$\begin{aligned} Z = X \times Y &= \sum_{k=0}^{M+N-1} Z_k 2^k \\ &= \left(\sum_{i=0}^{M-1} X_i 2^i \right) \left(\sum_{j=0}^{N-1} Y_j 2^j \right) = \sum_{i=0}^{M-1} \left(\sum_{j=0}^{N-1} X_i Y_j 2^{i+j} \right) \end{aligned} \quad (7.24)$$

KTH/ESDlab/HT

10/4/00

28

Binary multiplication

$$\begin{array}{r}
 101010 \\
 \times \quad 1011 \\
 \hline
 101010 \\
 000000 \\
 + \quad 101010 \\
 \hline
 111001110
 \end{array}$$

AND operation


Partial Products

KTH/ESDlab/HT

10/4/00

29

Indirect multiplication

 


1. Set $A = 0$
2. Read the LSB of Y register
3. AND it with the multiplicand X and add the result to Y
4. Store the sum to A and shift the contents of A and Y one bit right
5. Repeat 2. to 4. until all bits of the multiplier are handled
6. Read the result from A and Y registers

KTH/ESDlab/HT

10/4/00

30

Array multiplier

 


KTH/ESDlab/HT

10/4/00

31

MxN array multiplier critical path

 


$$t_{mult} = [(M-1) + (N-2)]t_{carry} + (N-1)t_{sum} + (N-1)t_{and}$$

KTH/ESDlab/HT

10/4/00

32

 Carry ripple vs. carry save array multiplier




KTH/ESDlab/HT

10/4/00

33

Carry save multiplier

 


$$t_{mult} = (N-1)t_{carry} + (N-1)t_{and} + t_{merge}$$

KTH/ESDlab/HT

10/4/00

34

Adder cells in array multiplier

 


Identical Delays for Carry and Sum

KTH/ESDlab/HT

10/4/00

35

Array multiplier floorplan

 

KTH/ESDlab/HT

10/4/00

36

Wallace tree multiplier

 



FIGURE 2.29 A 6-bit Wallace-tree multiplier. The carry-save adder (CSA) requires 26 adders (cells 1–26, six are half adders). The final carry-propagate adder (CPA) consists of 4 adder cells (27–30). The delay of the CSA is 6 adders. The delay of the CPA is 4 adders.

KTH/ESDlab/HT

10/4/00

37

Wallace tree multiplier

 


KTH/ESDlab/HT

10/4/00

38

Wallace tree multiplier

 

KTH/ESDlab/HT

10/4/00

39

Dadda tree multiplier

 



FIGURE 2.30 The 6-bit Dadda multiplier. The carry-save adder (CSA) requires 20 adders (cells 1–20, four are half adders). The carry-propagate adder (CPA, cells 21–30) is a ripple-carry adder (RCA). The CSA is smaller (20 versus 26 adders), faster (3 adder delays versus 6 adder delays), and more regular than the Wallace-tree CSA of Figure 2.29. The overall speed of this implementation is approximately the same as the Wallace-tree multiplier of Figure 2.29; however, the speed may be increased by substituting a faster CPA.

KTH/ESDlab/HT

10/4/00

40

Serial-serial multiplier

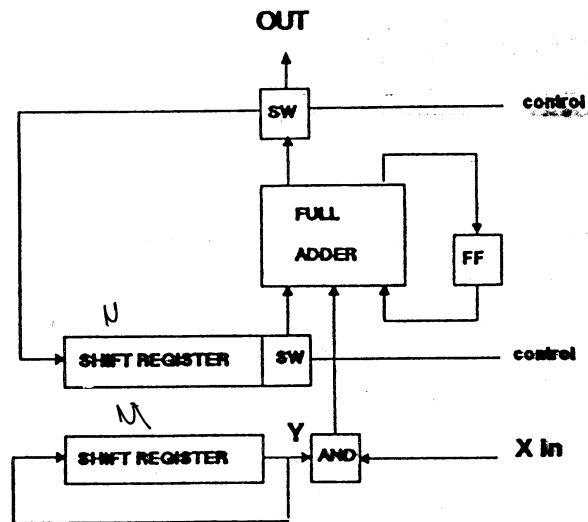


KTH/ESDlab/HT

10/4/00

41

Serial-parallel multiplier

 


KTH/ESDlab/HT

10/4/00

42

Parallel vs. serial multipliers

 


KTH/ESDlab/HT

10/4/00

43

Parallel vs. serial multipliers

 

KTH/ESDlab/HT

10/4/00

44

Multiplier performance

MULTIPLICAND	MULTIPLIER	CLOCK PULSES	FULL ADDERS	AND-GATES
parallel	parallel	1	n^2	n^2
parallel	serial	n	n	n
serial	parallel	$2n$	n	n
serial	serial	$n(n+1)$ or $2n^2$	1	1

KTH/ESDlab/HT

10/4/00

45

Multiplier performance

Multiplier type	N×N	8×8	16×16	32×32
Indirect with RCA	$(2N+2)NT$	144T	544T	2112T
Linear array with RCA	$(4N-2)T$	30T	62T	126T
Linear array with CLA	$(2N+8)T$	24T	40T	72T
Wallace tree with CLA	$(2M+8)T$	16T	20T	24T
Pipelined *) linear array	$> 2T$	$> 2T$	$> 2T$	$> 2T$
Logarithmic with CLA	$2T(m)+8T$	$2T(m)+8T$	---	---

N is the input word length
M is the number of FA stages in Wallace tree structure
T is the basic gate delay
T(m) is the ROM access time in logarithmic multiplier

Assumed delays in this table:

Full adder delay 2T
CLA delay 8T

*) 1/throughput values are considered in this table

KTH/ESDlab/HT

10/4/00

46


Multiplier summary

- **Optimization Goals Different Vs Binary Adder**
- **Once Again: Identify Critical Path**
- **Other possible techniques**
 - **Logarithmic versus Linear (Wallace Tree Mult)**
 - **Data encoding (Booth)**
 - **Pipelining**

FIRST GLIMPSE AT SYSTEM LEVEL OPTIMIZATION

Other datapath elements

Binary shifter

 


KTH/ESDlab/HT

10/4/00

49

Barrel shifter

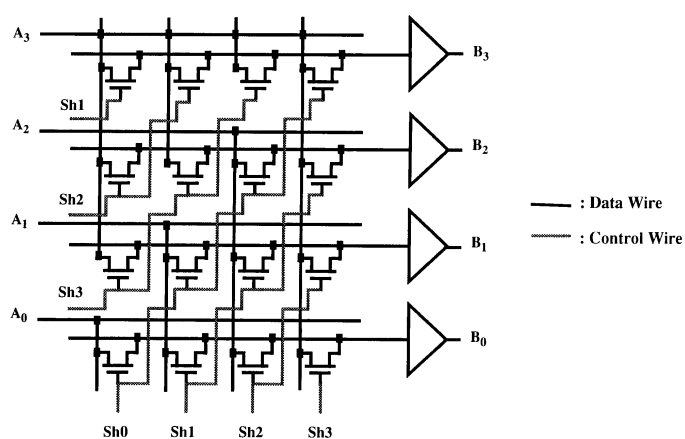


Area dominated by Wiring!

KTH/ESDlab/HT

10/4/00

50

4x4 barrel shifter

 


KTH/ESDlab/HT

10/4/00

51

Logarithmic shifter

 

KTH/ESDlab/HT

10/4/00

52

Power considerations in datapath structures

KTH/ESDlab/HT

10/4/00

53

Reducing supply voltage

An architectural approach

- Operate at lowest supply voltage at lowest possible speed!
- Use Architecture optimization to compensate for slower operation.
e.g. Concurrency, Pipelining



Trade-off AREA for lower POWER

KTH/ESDlab/HT

10/4/00

54

Reducing supply voltage

 



Figure 4.56 Normalized propagation delay as a function of supply voltage for a number of experimental circuits.

KTH/ESDlab/HT

10/4/00

55

 Architecture trade-offs: reference datapath




- Critical path delay $\Rightarrow T_{\text{adder}} + T_{\text{comparator}} (= 25\text{ns})$
 $\Rightarrow f_{\text{ref}} = 40\text{Mhz}$
- Total capacitance being switched = C_{ref}
- $V_{\text{dd}} = V_{\text{ref}} = 5\text{V}$
- Power for reference datapath = $P_{\text{ref}} = C_{\text{ref}} V_{\text{ref}}^2 f_{\text{ref}}$

KTH/ESDlab/HT

10/4/00

56

Parallel datapath

 


- The clock rate can be reduced by half with the same throughput $\Rightarrow f_{\text{par}} = f_{\text{ref}} / 2$
- $V_{\text{par}} = V_{\text{ref}} / 1.7$, $C_{\text{par}} = 2.15 C_{\text{ref}}$
- $P_{\text{par}} = (2.15 C_{\text{ref}}) (V_{\text{ref}}/1.7)^2 (f_{\text{ref}}/2) \approx 0.36 P_{\text{ref}}$

KTH/ESDlab/HT

10/4/00

57

Pipelined datapath

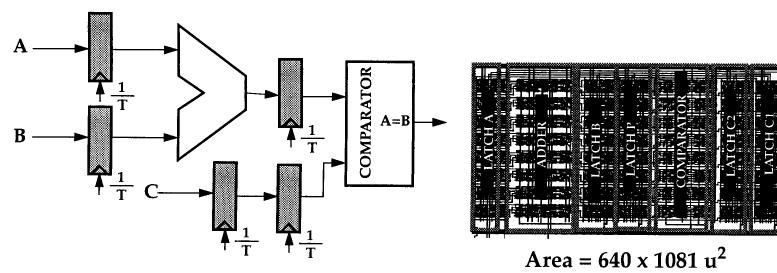

- $f_{\text{pipe}} = f_{\text{ref}}$
 $C_{\text{pipe}} = 1.1 C_{\text{ref}}$
 $V_{\text{pipe}} = V_{\text{ref}}/1.7$
- Voltage can be dropped while maintaining the original throughput.
- $P_{\text{pipe}} = C_{\text{pipe}} V_{\text{pipe}}^2 f_{\text{pipe}} = (1.1 C_{\text{ref}}) (V_{\text{ref}}/1.7)^2 f_{\text{ref}} = 0.37 P_{\text{ref}}$

KTH/ESDlab/HT

10/4/00

58

Datapath architecture summary



Architecture type	Voltage	Area	Power
Simple datapath (no pipelining or parallelism)	5V	1	1
Pipelined datapath	2.9V	1.3	0.37
Parallel datapath	2.9V	3.4	0.34
Pipeline-Parallel	2.0V	3.7	0.18

KTH/ESDlab/HT

10/4/00

59

Glitching in NOR chain

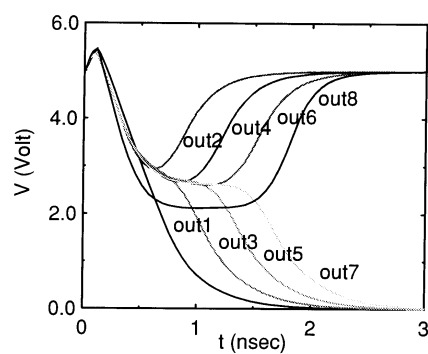 


KTH/ESDlab/HT

10/4/00

60

Glitching in RCA

 

KTH/ESDlab/HT


10/4/00

61

Switching activity in adders

Power-Delay-Product⁻¹

	16 bit	32 bit	64 bit
Ripple Carry	3.09	0.81	0.27
Carry Lookahead	10.0	3.54	1.76
Carry Bypass	5.45	2.39	0.99
Carry Select	4.44	2.08	1.00
Conditional Sum	3.82	1.23	0.42

 

Logic Transition Histogram

from Callaway & Swartzlander

KTH/ESDlab/HT


10/4/00

62

Switching activity in multipliers

Power-Delay-Product⁻¹

	8 bit	16 bit	32 bit
Array	32.01	1.15	0.04
Wallace	49.86	5.06	0.81
Dadda	51.3	5.79	0.95

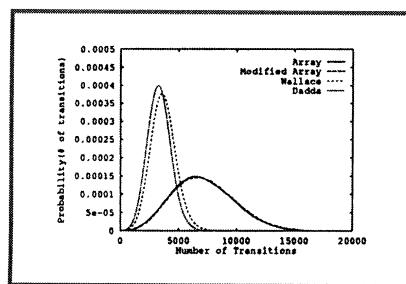

Logic Transition Histogram


from Callaway & Swartzlander

KTH/ESDlab/HT

10/4/00

63

Layout strategy for datapath

 

KTH/ESDlab/HT

10/4/00


64

Layout strategy for datapaths

(a) Datapath without feedthroughs and without pitch matching (area = 4.2 mm^2).

(b) Adding feedthroughs (area = 3.2 mm^2)

 (c) Equalizing the cell height reduces the area to 2.2 mm^2 .




KTH/ESDlab/HT

10/4/00

65

Cell area: 2 vs. 3 metal layer process

 

KTH/ESDlab/HT

10/4/00

66

Summary

1. The most important message is to select the *right structure* before starting an elaborate circuit optimization. Going for the optimal performance of a complex structure by rigorously optimizing transistor sizes and topologies might not always be the best choice. Optimizations at higher levels of abstraction, such as the logic level, can often generate more dramatic results. Simple first-order calculations can help give a global picture on the pros and cons of a proposed structure.
2. Determine the *critical timing path* through the circuit and focus most of your optimization efforts on that part of the circuit. Computer-aided design tools are available to help determine the critical paths and size the transistors appropriately.
3. Circuit size is not always determined by the number of transistors, but also by other factors such as *wiring and the number of vias and contacts*. These factors are becoming even more important with shrinking dimensions or when extreme performance is a goal, as will become obvious in the next chapter.
4. Although an obscure optimization can sometimes help to get a better result, be wary if this results in an irregular and convoluted topology. *Regularity and modularity* are a designer's best friend.